



THE PROCESSOR

Prof. Sebastian Eslava Ph.D.

Introduction

- CPU performance factors
 - Instruction count
 - Determined by ISA and compiler
 - CPI and Cycle time
 - Determined by CPU hardware
- We will examine two MIPS implementations
 - A simplified version (Single-cycle and multi-cycle)
 - A more realistic pipelined version
- Simple subset, shows most aspects
 - Memory reference: lw, sw
 - Arithmetic/logical: add, sub, and, or, slt
 - Control transfer: beq, j


Instruction Execution

- PC \rightarrow instruction memory, fetch instruction
- Register numbers \rightarrow register file, read registers
- Depending on instruction class
 - Use ALU to calculate
 - Arithmetic result
 - Memory address for load/store
 - Branch target address
 - Access data memory for load/store
 - PC \leftarrow target address or PC + 4

Building a Datapath


- Datapath
 - Elements that process data and addresses in the CPU
 - Registers, ALUs, mux's, memories, ...
- We will build a MIPS datapath incrementally
 - Refining the overview design

Instruction Fetch

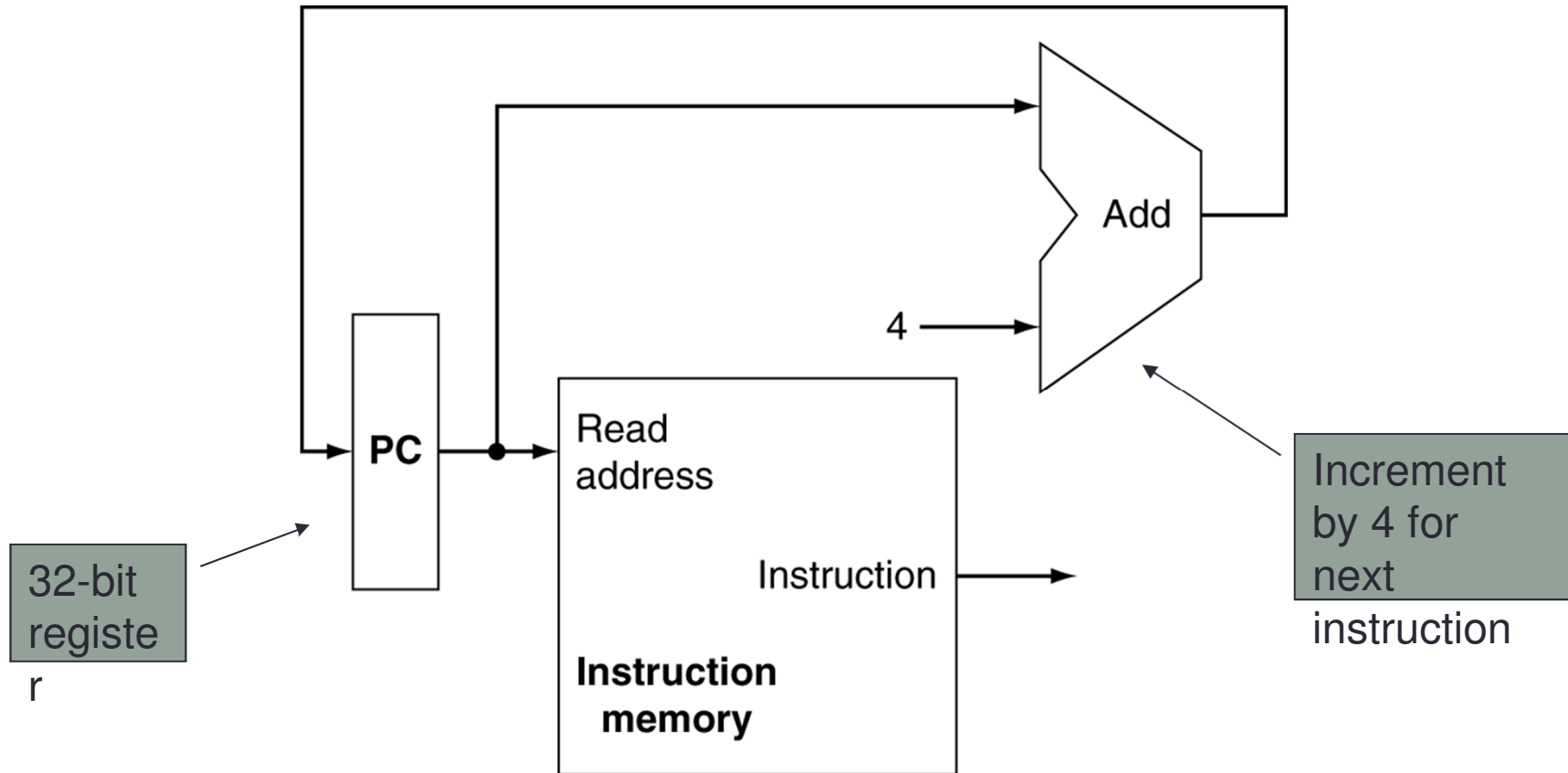


R-Format Instructions

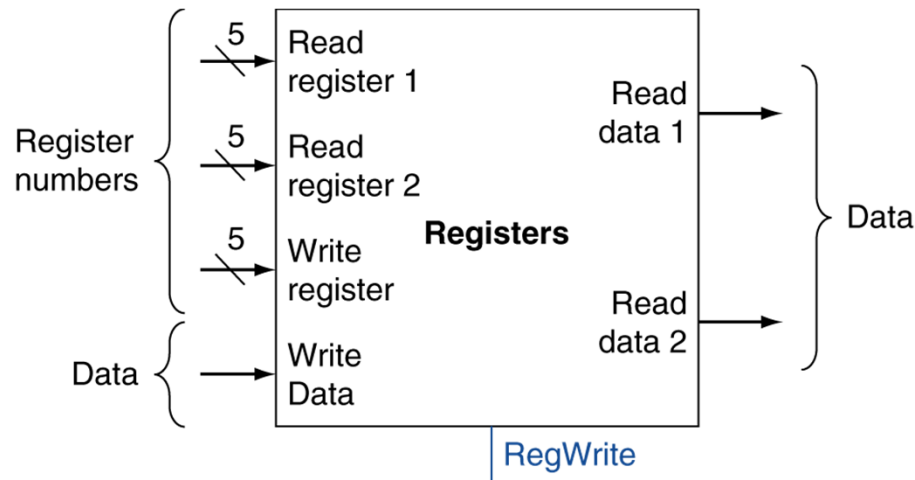- Read two register operands
- Perform arithmetic/logical operation
- Write register result




a. Registers

 

 
b. ALU

Load/Store Instructions

- Read register operands
- Calculate address using 16-bit offset
 - Use ALU, but sign-extend offset
- Load: Read memory and update register
- Store: Write register value to memory



a. Data memory unit

 


b. Sign extension unit

Branch Instructions


- Read register operands
- Compare operands
 - Use ALU, subtract and check Zero output
- Calculate target address
 - Sign-extend displacement
 - Shift left 2 places (word displacement)
 - Add to PC + 4
 - Already calculated by instruction fetch

Branch Instructions

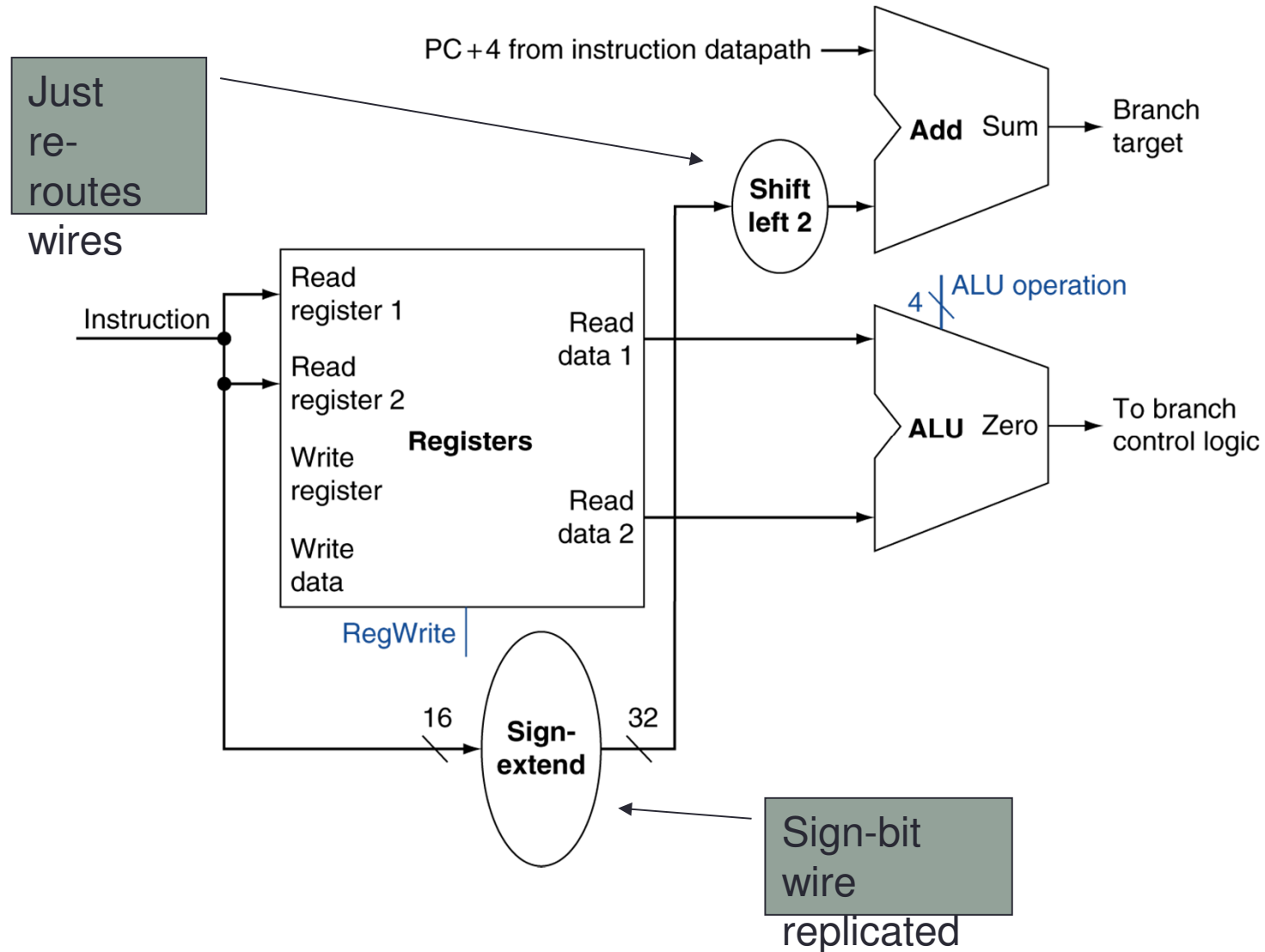


Single-Cycle MIPS Processor

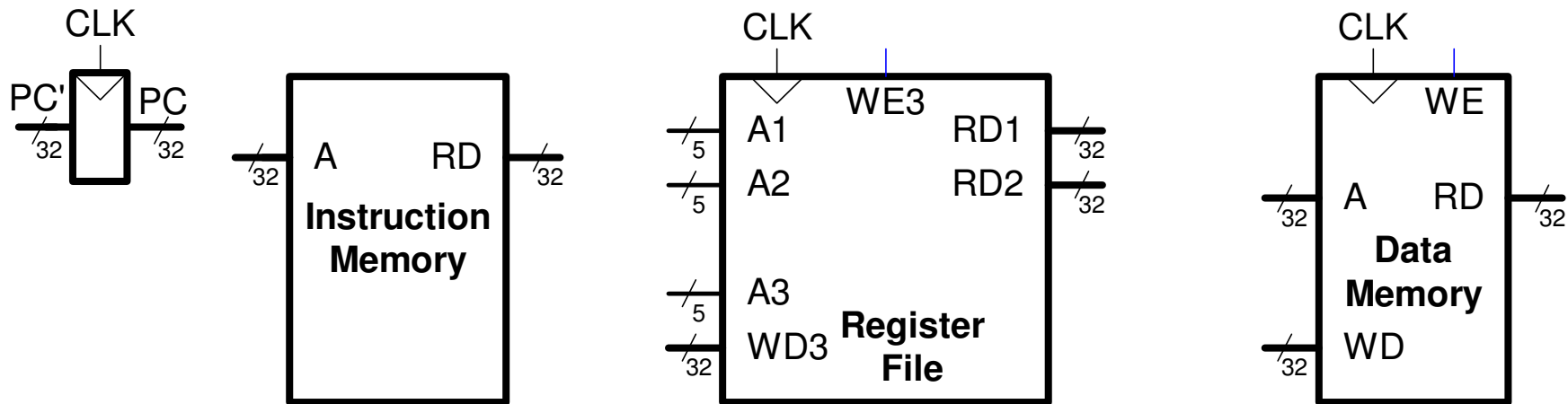- Each instruction executes in a single cycle
- Components:
 - Datapath
 - Control




Single-Cycle Datapath: 1_w fetch

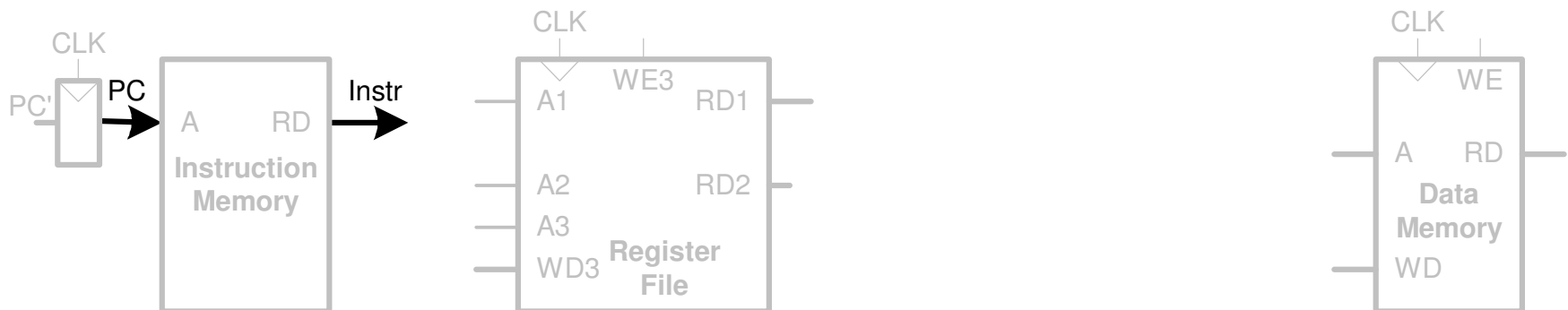- First consider executing 1_w
- **STEP 1:** Fetch instruction




Single-Cycle Datapath: lw register read

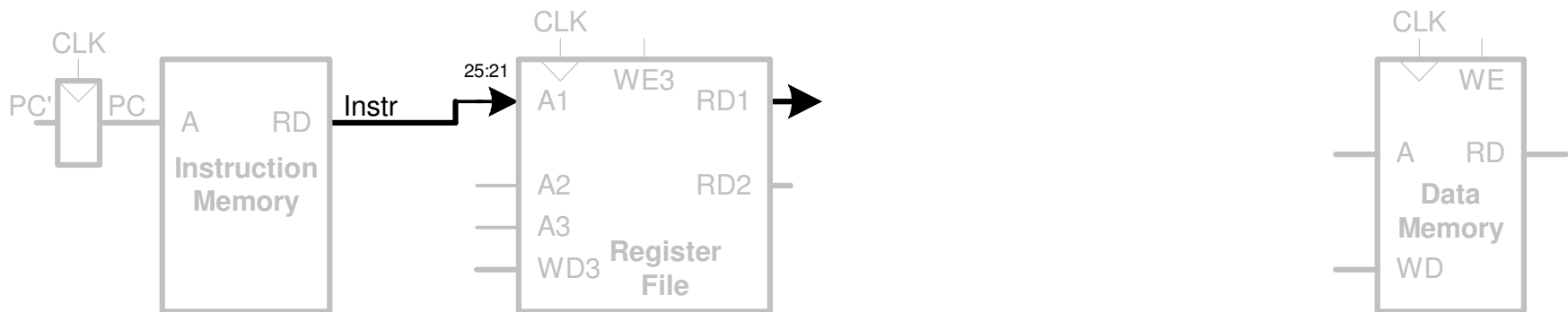- **STEP 2:** Read source operands from register file




Single-Cycle Datapath: lw immediate

- **STEP 3:** Sign-extend the immediate

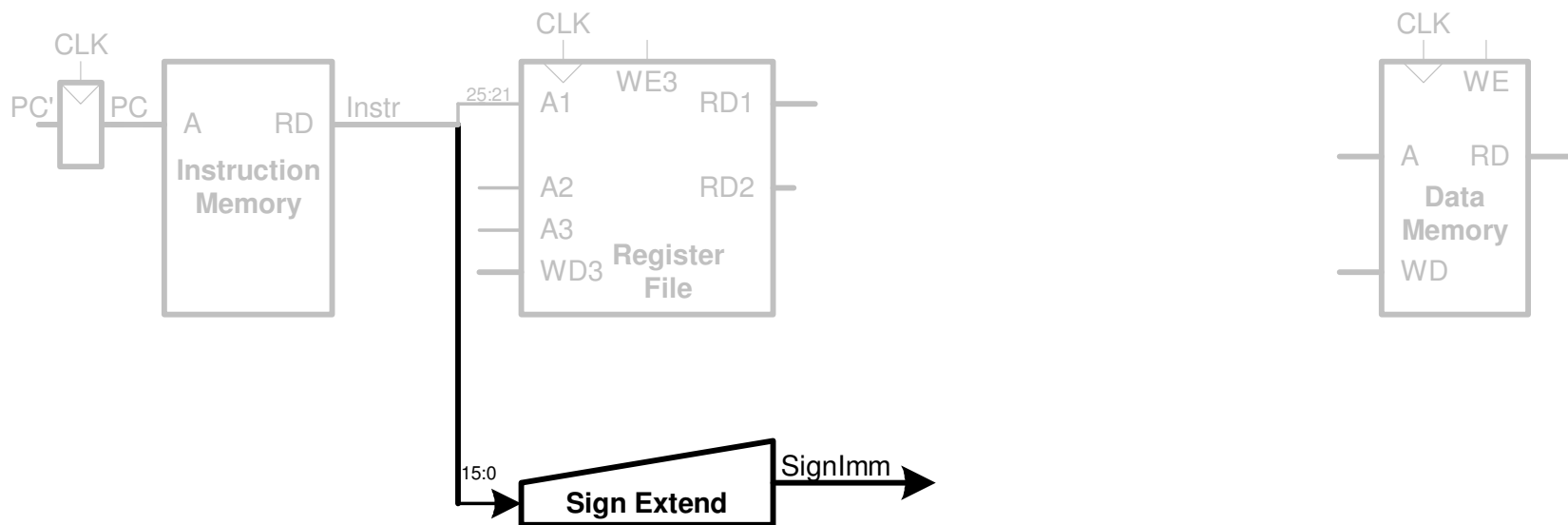


Single-Cycle Datapath: lw address

- **STEP 4:** Compute the memory address

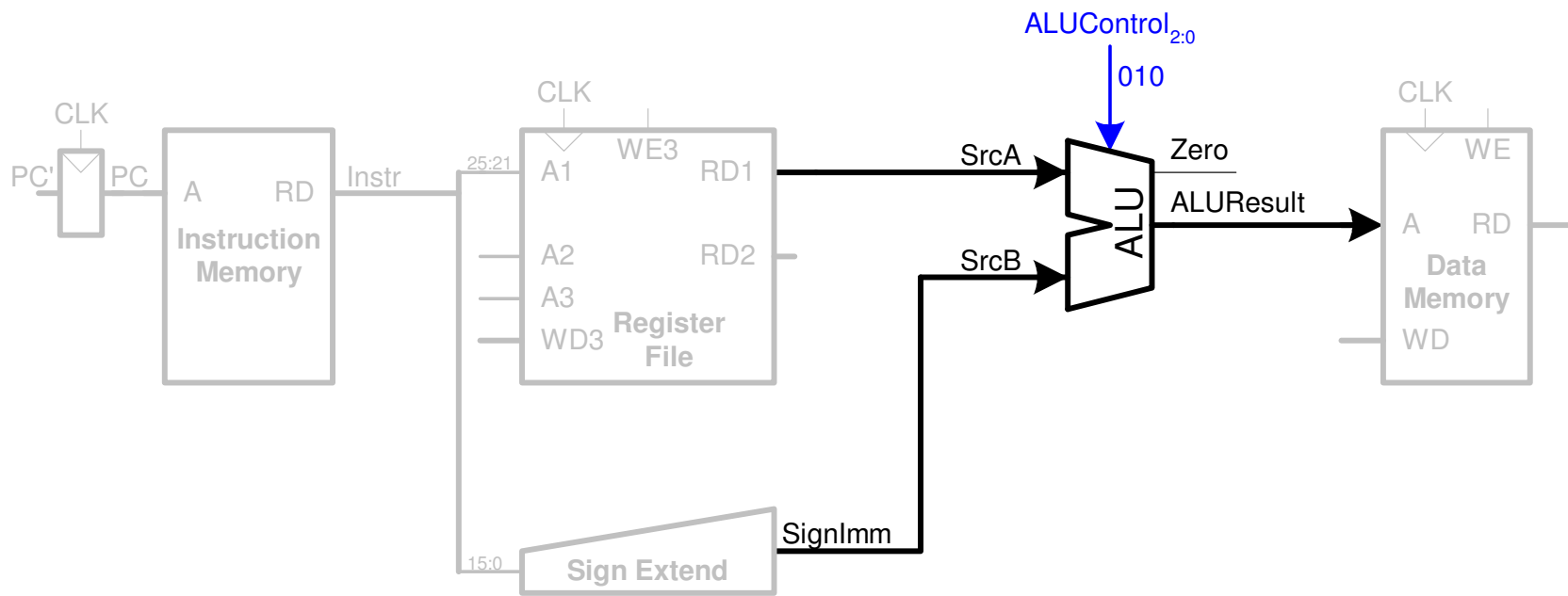


Single-Cycle Datapath: lw memory read

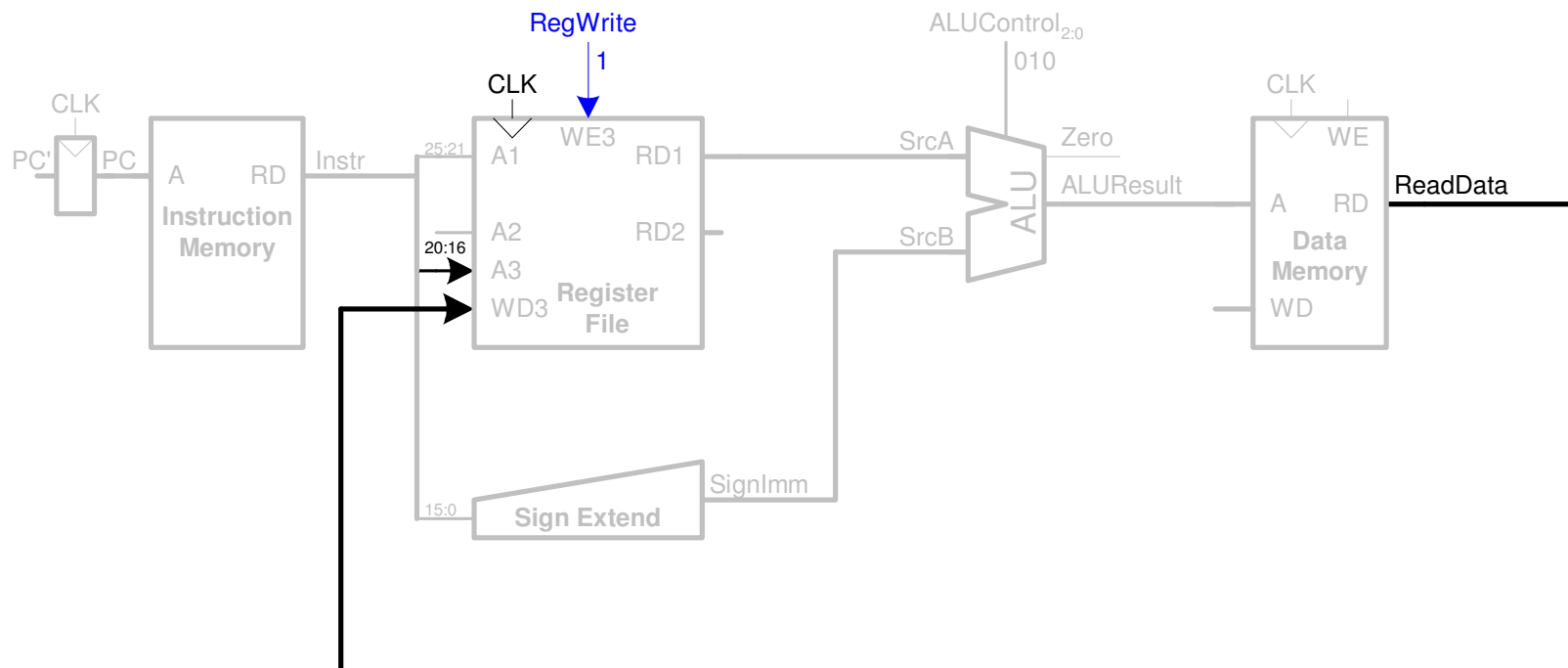- **STEP 5:** Read data from memory and write it back to register file




Single-Cycle Datapath: lw PC increment

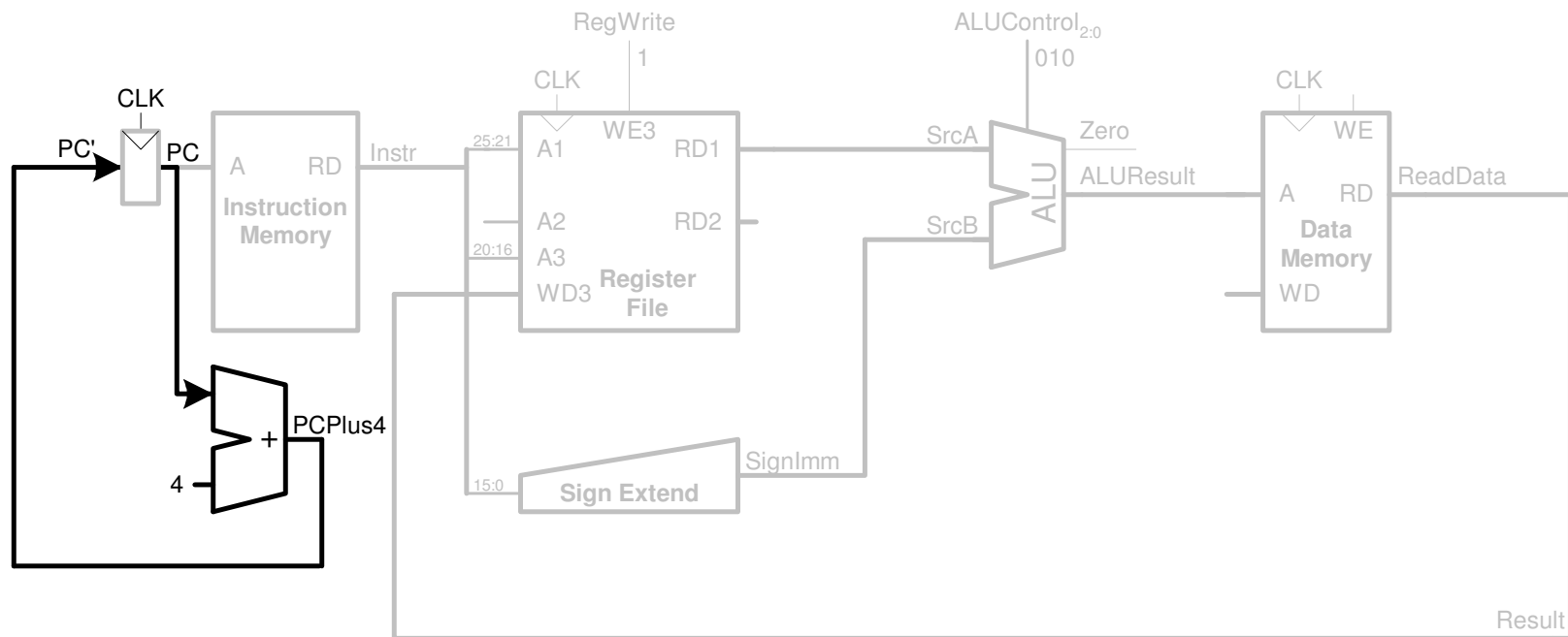- **STEP 6:** Determine the address of the next instruction




Single-Cycle Datapath: sw

- Write data in `rt` to memory

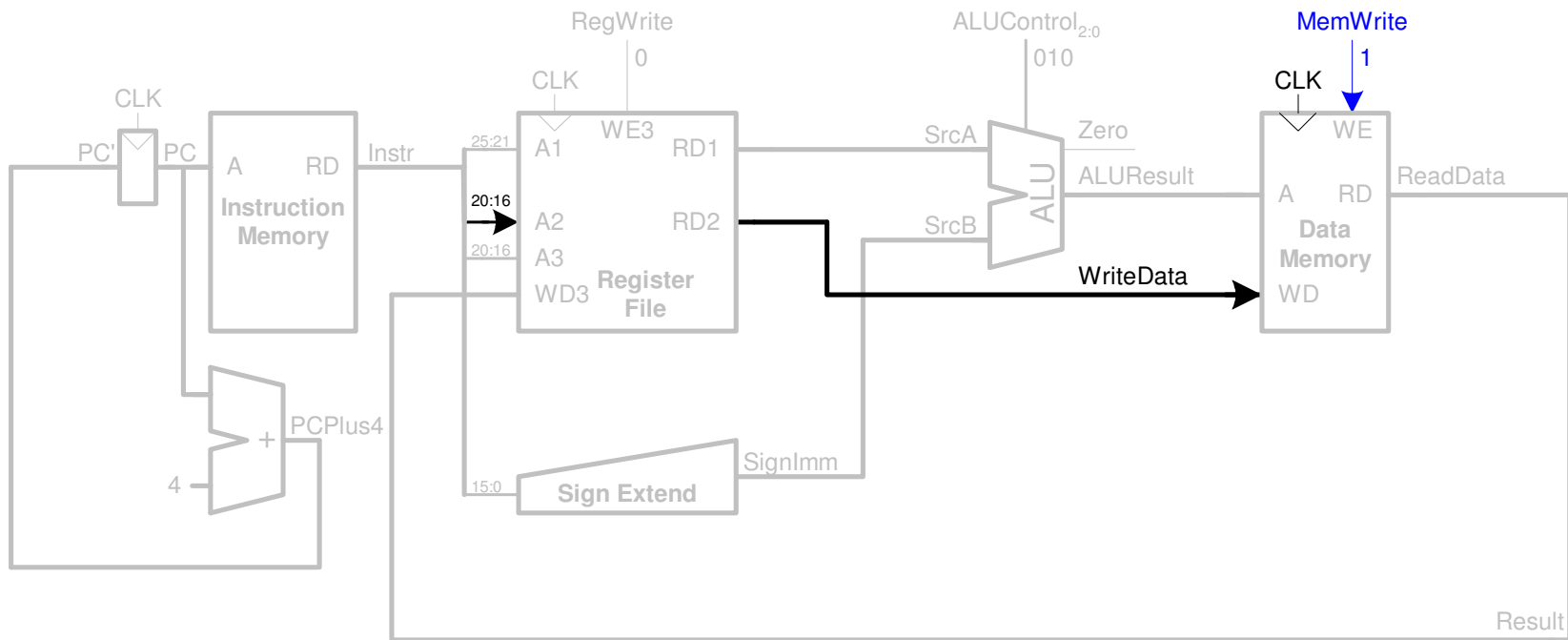

Single-Cycle Datapath: R-type instructions

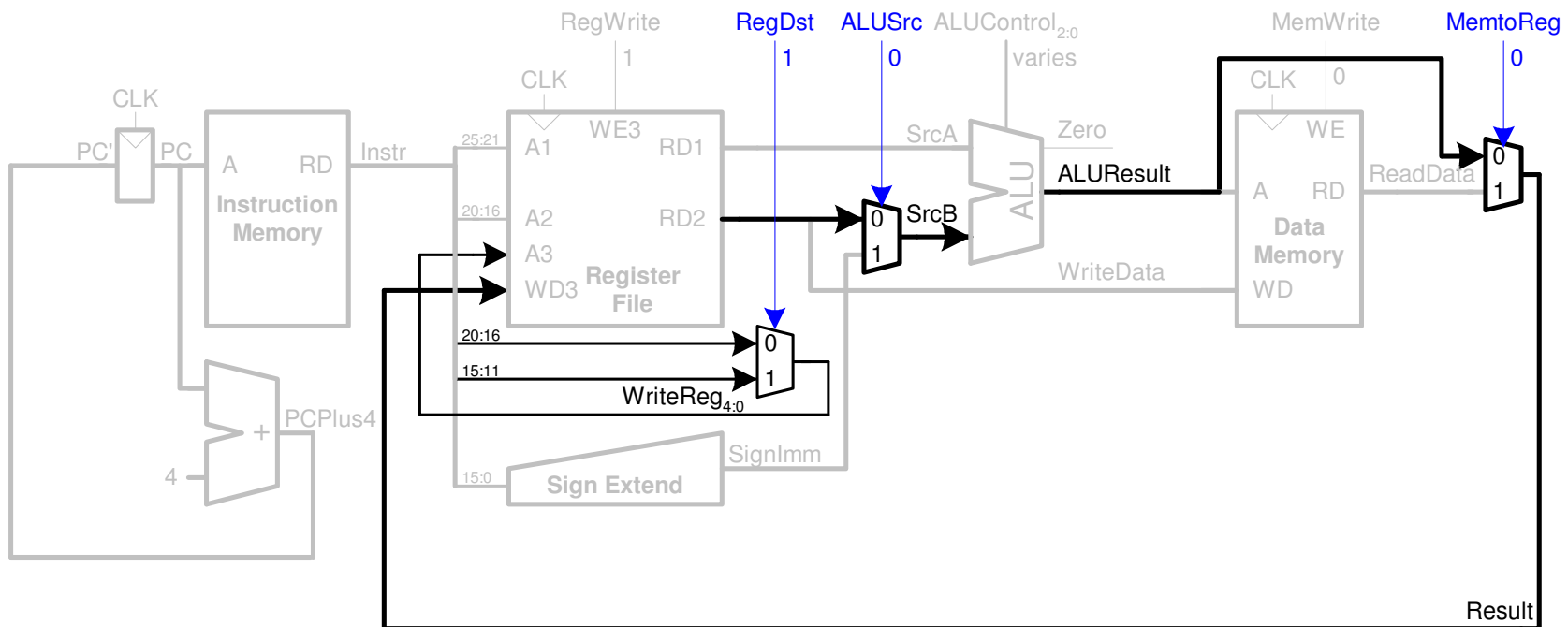
- Read from `rs` and `rt`
- Write *ALUResult* to register file
- Write to `rd` (instead of `rt`)




Single-Cycle Datapath: beq

- Determine whether values in r_s and r_t are equal
- Calculate branch target address:

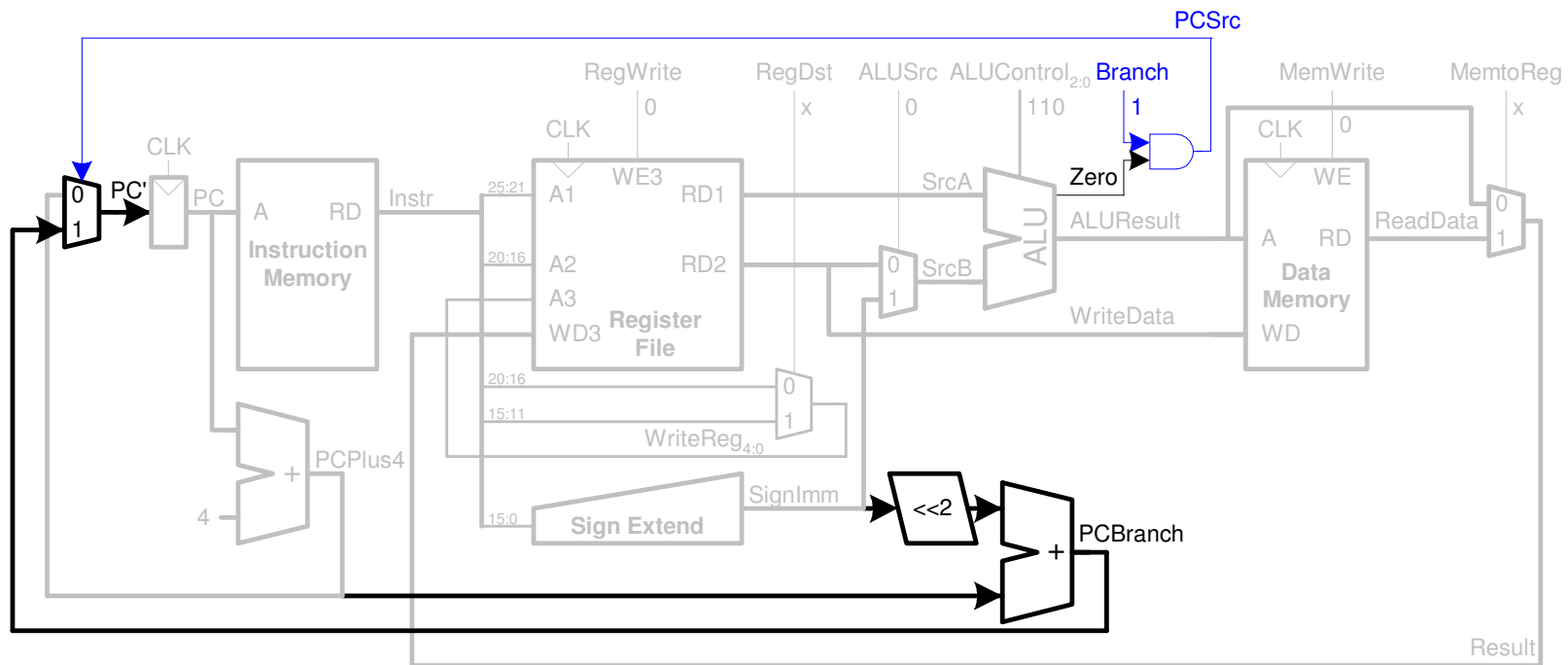
$$\text{BTA} = (\text{sign-extended immediate} \ll 2) + (\text{PC} + 4)$$




Complete Single-Cycle Processor

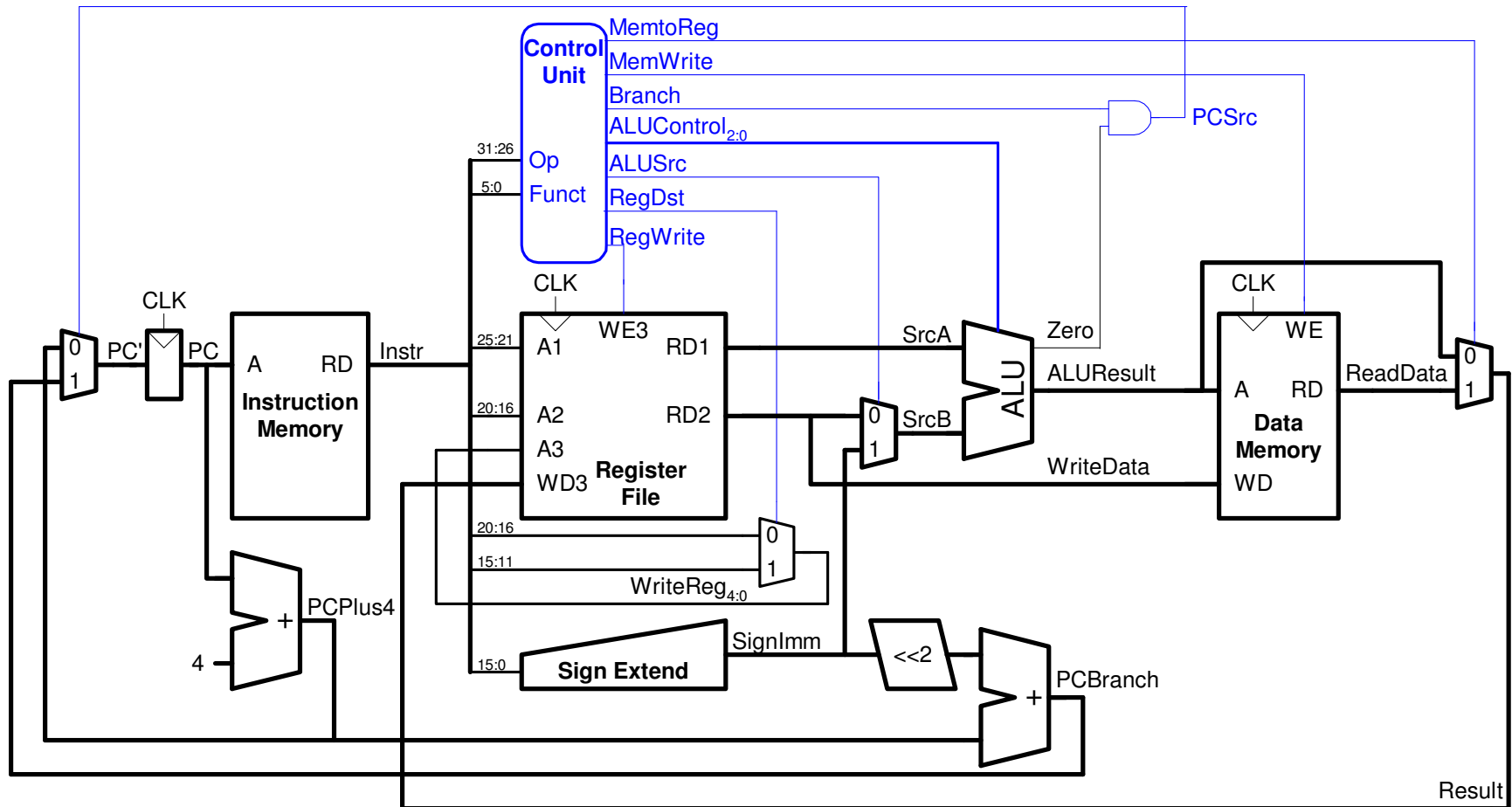

Control Unit

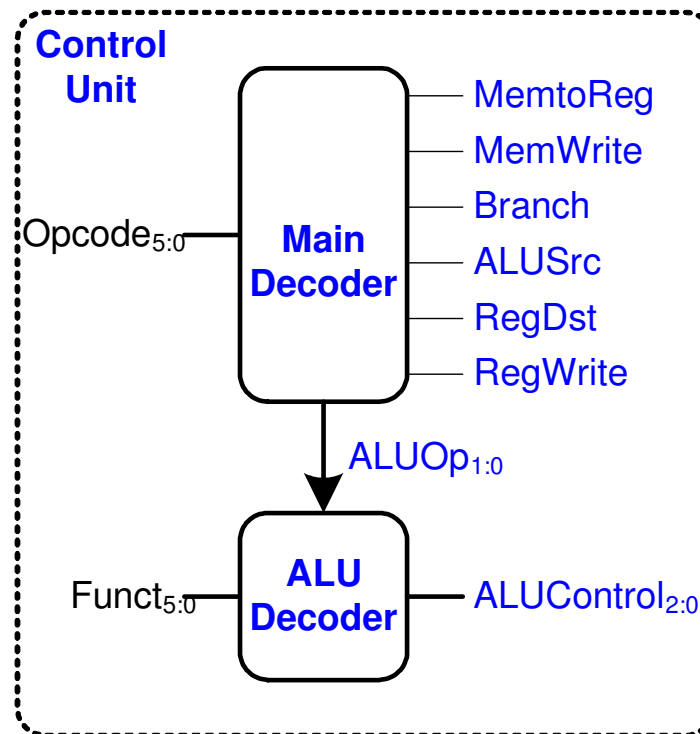

Review: ALU

 

$F_{2:0}$	Function
000	A & B
001	A B
010	A + B
011	not used
100	A & ~B
101	A ~B
110	A - B
111	SLT


Control Unit: ALU Decoder

ALUOp_{1:0}	Meaning
00	Add
01	Subtract
10	Look at Funct
11	Not Used


ALUOp_{1:0}	Funct	ALUControl_{2:0}
00	X	010 (Add)
X1	X	110 (Subtract)
1X	100000 (add)	010 (Add)
1X	100010 (sub)	110 (Subtract)
1X	100100 (and)	000 (And)
1X	100101 (or)	001 (Or)
1X	101010 (slt)	111 (SLT)

Control Unit: Main Decoder

Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemtoReg	ALUOp _{1:0}
R-type	000000	1	1	0	0	0	0	10
lw	100011	1	0	1	0	0	1	00
sw	101011	0	X	1	0	1	X	00
beq	000100	0	X	0	1	0	X	01

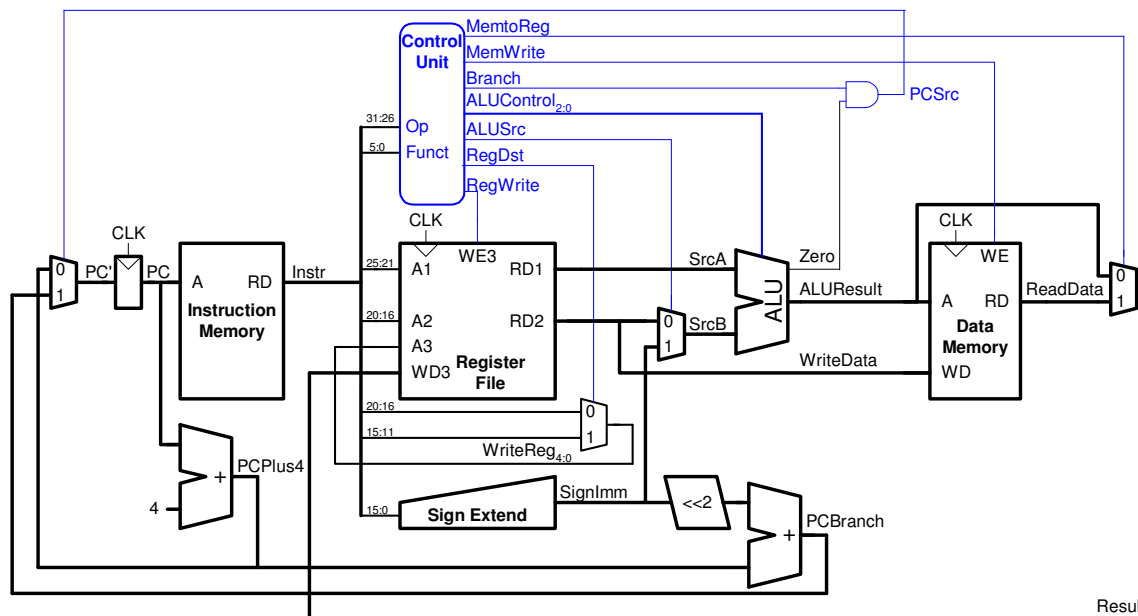


Single-Cycle Datapath Example: or

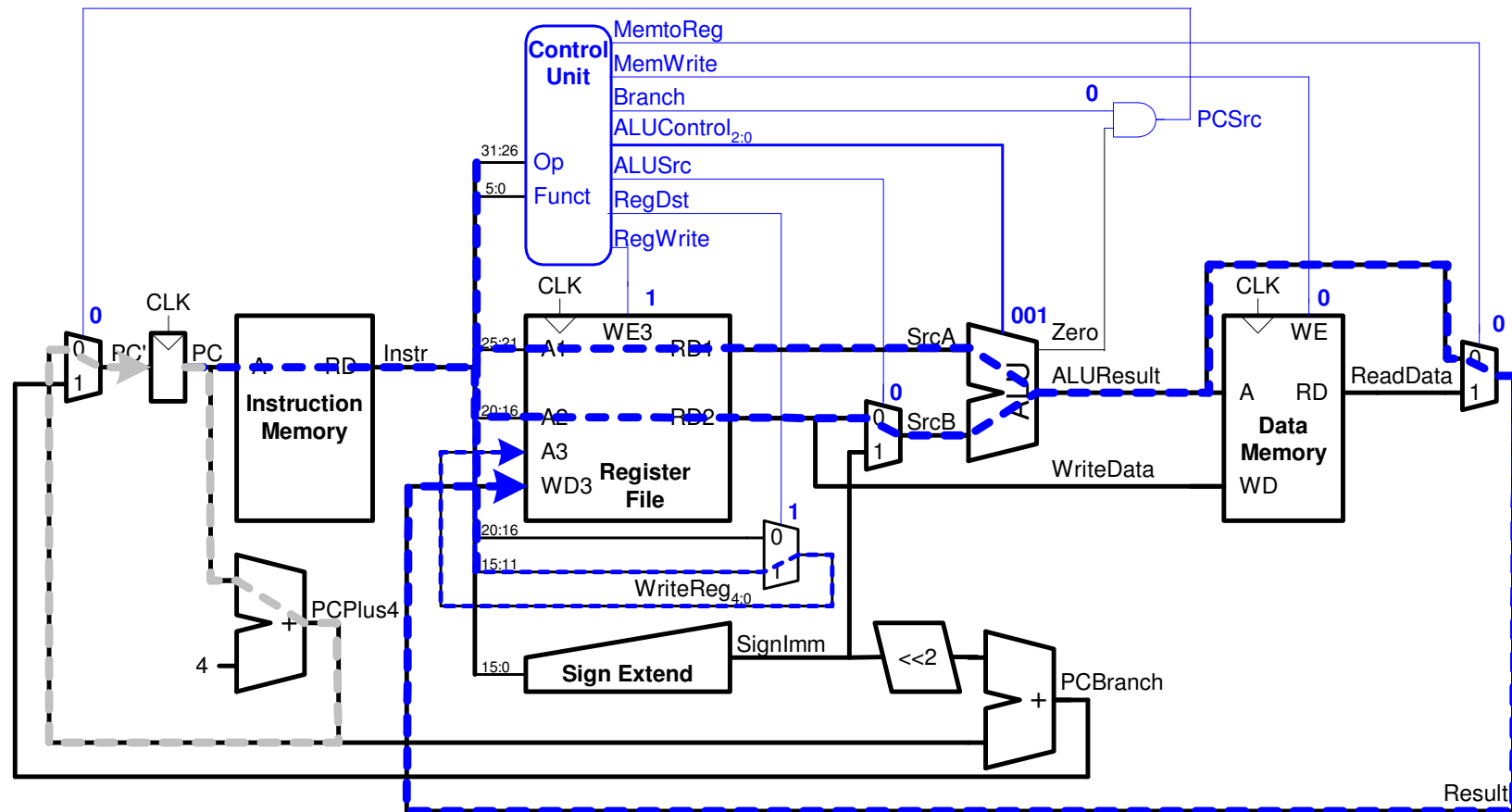

Extended Functionality: addi


- No change to datapath

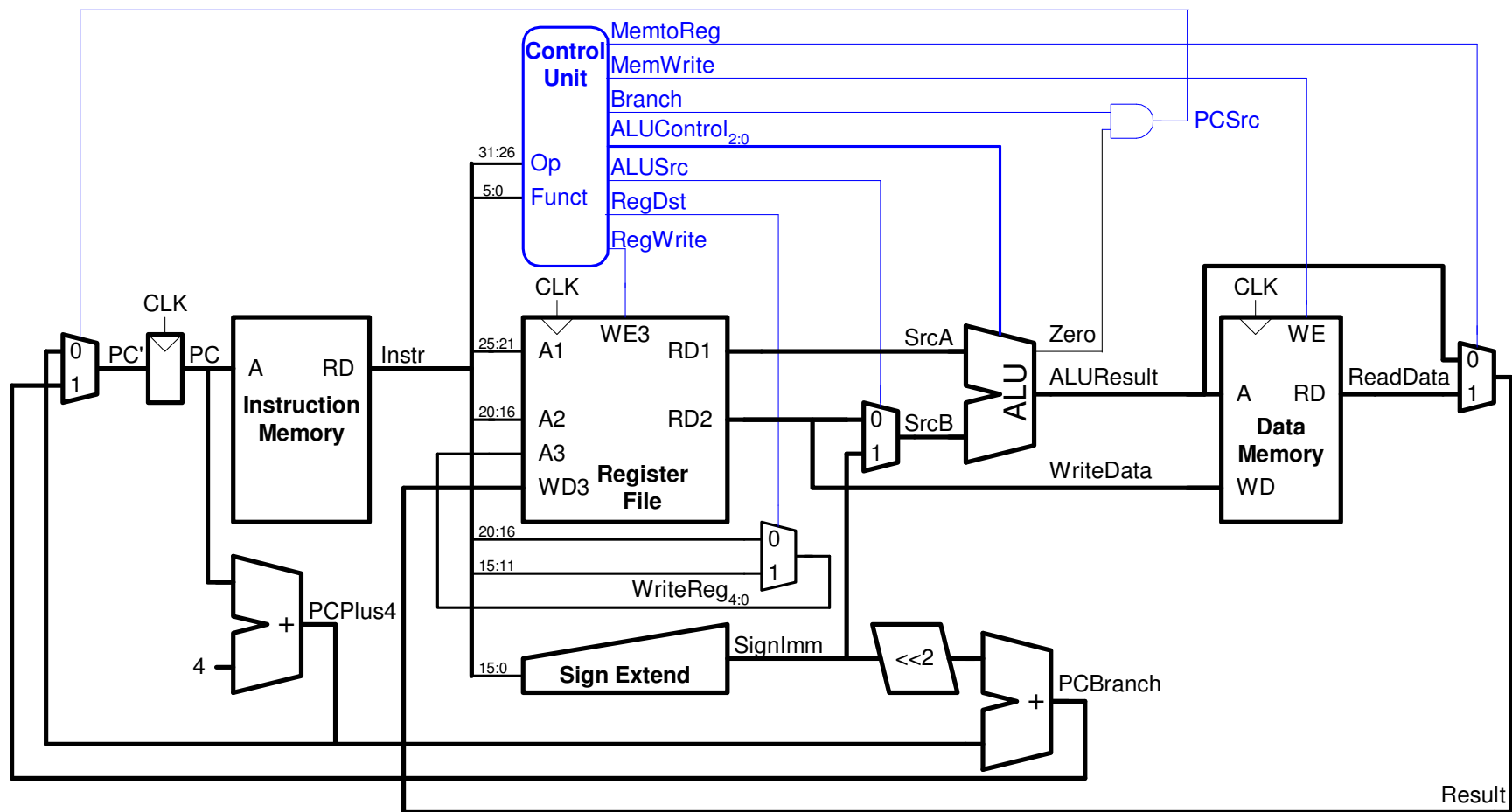

Control Unit: *addi*

Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemtoReg	ALUOp _{1:0}
R-type	000000	1	1	0	0	0	0	10
lw	100011	1	0	1	0	0	1	00
sw	101011	0	X	1	0	1	X	00
beq	000100	0	X	0	1	0	X	01
<i>addi</i>	<i>001000</i>	<i>1</i>	<i>0</i>	<i>1</i>	<i>0</i>	<i>0</i>	<i>0</i>	<i>00</i>

Extended Functionality: j

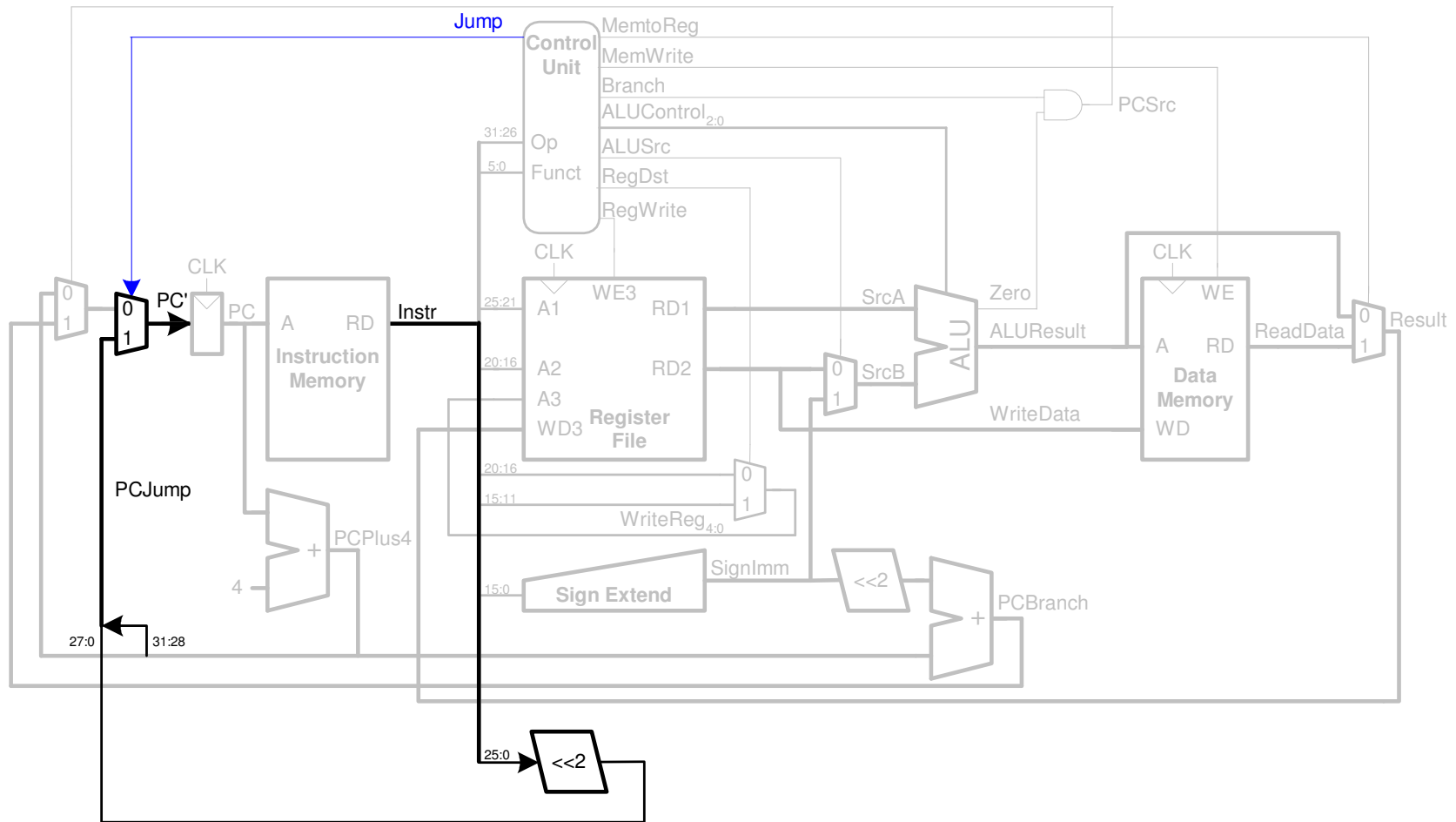

Control Unit: Main Decoder

Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemtoReg	ALUOp _{1:0}	Jump
R-type	000000	1	1	0	0	0	0	10	0
lw	100011	1	0	1	0	0	1	00	0
sw	101011	0	X	1	0	1	X	00	0
beq	000100	0	X	0	1	0	X	01	0
j	000010	0	X	X	X	0	X	XX	1


Review: Processor Performance

Program Execution Time

$$\begin{aligned} &= (\# \\ &\text{instructions})(\text{cycles/instruction})(\text{seconds/cycle}) \\ &= \# \text{ instructions} \times \text{CPI} \times T_c \end{aligned}$$

Single-Cycle Performance

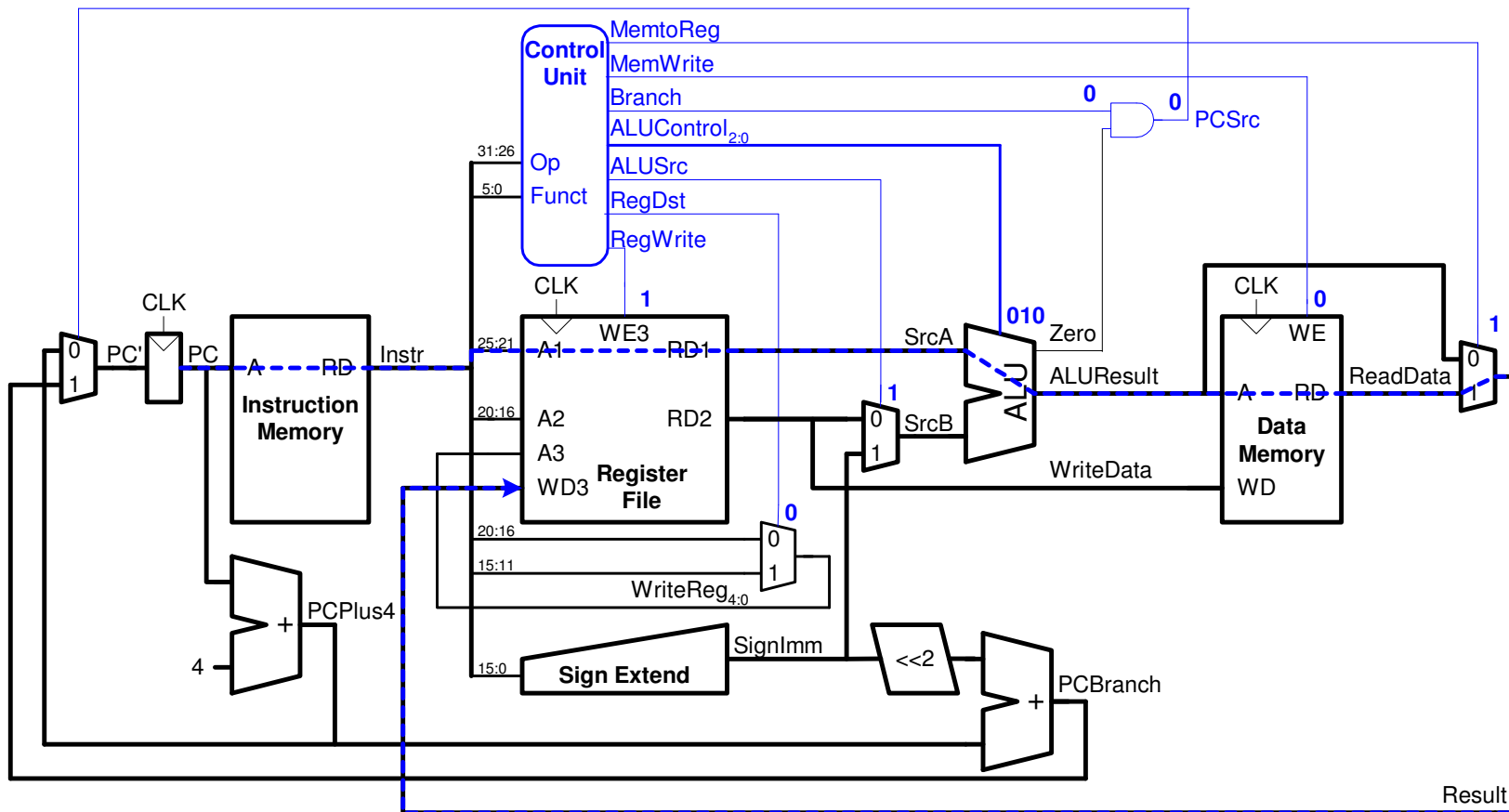- T_C is limited by the critical path (1w)



Single-Cycle Performance

- Single-cycle critical path:

$$T_c = t_{pcq_PC} + t_{\text{mem}} + \max(t_{RF\text{read}}, t_{\text{sext}} + t_{\text{mux}}) + t_{\text{ALU}} + t_{\text{mem}} + t_{\text{mux}} + t_{RF\text{setup}}$$

- In most implementations, limiting paths are:

- memory, ALU, register file.

- $T_c = t_{pcq_PC} + 2t_{\text{mem}} + t_{RF\text{read}} + t_{\text{mux}} + t_{\text{ALU}} + t_{RF\text{setup}}$

Single-Cycle Performance Example

Element	Parameter	Delay (ps)
Register clock-to-Q	t_{pcq_PC}	30
Register setup	t_{setup}	20
Multiplexer	t_{mux}	25
ALU	t_{ALU}	200
Memory read	t_{mem}	250
Register file read	t_{RFread}	150
Register file setup	$t_{RFsetup}$	20

$$\begin{aligned}T_c &= t_{pcq_PC} + 2t_{mem} + t_{RFread} + t_{mux} + t_{ALU} + t_{RFsetup} \\&= [30 + 2(250) + 150 + 25 + 200 + 20] \text{ ps} \\&= 925 \text{ ps}\end{aligned}$$

Single-Cycle Performance Example

- For a program with 100 billion instructions executing on a single-cycle MIPS processor,

$$\begin{aligned}\text{Execution Time} &= \# \text{ instructions} \times \text{CPI} \times T_C \\ &= (100 \times 10^9)(1)(925 \times 10^{-12} \text{ s}) \\ &= 92.5 \text{ seconds}\end{aligned}$$