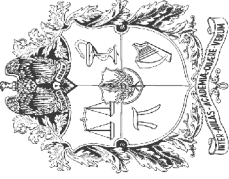


## 2012-1: Transmission Lines and Antennas




Javier Leonardo Araque Quijano  
Of: 453 – 204  
Ext. 14083  
jlaraqueq@unal.edu.co

1
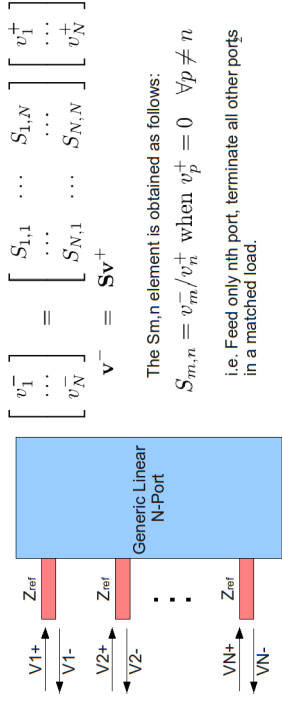
## Scattering Matrix

The Scattering Matrix (S-Matrix) is the preferred representation at microwave frequencies as voltage/currents are not well defined in all cases as required for usual matrix representations ( $Z$ ,  $Y$ , etc.)



## Properties of the S-Matrix

$\mathbf{S} = \mathbf{S}^T$  for reciprocal networks

$\sum_{k=1}^N |S_{k,n}|^2 \leq 1 \quad \forall n$  for passive networks  
 i.e. norm of column vectors is always  $\leq 1$   
 (equality holds for lossless networks)


$$\mathbf{S} = (\mathbf{Z}/Z_0 + \mathbf{I})^{-1} (\mathbf{Z}/Z_0 - \mathbf{I}) \quad \mathbf{Z} = Z_0 (\mathbf{I} + \mathbf{S}) (\mathbf{I} - \mathbf{S})^{-1}$$

$$\mathbf{S} = (\mathbf{I} + \mathbf{Y}/Y_0)^{-1} (\mathbf{I} - \mathbf{Y}/Y_0) \quad \mathbf{Y} = Y_0 (\mathbf{I} - \mathbf{S}) (\mathbf{I} + \mathbf{S})^{-1}$$

where  $\mathbf{Z}$  and  $\mathbf{Y}$  are the impedance and admittance matrices,  
 $\mathbf{I}$  is the identity matrix and  $Z_0$  and  $Y_0$  are the port reference impedance/admittance.
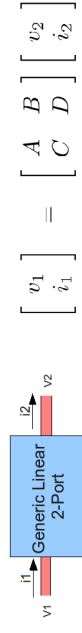
## The ABCD matrix

- 2-ports are probably the most common device.
- These are usually cascaded.
- ABCD matrix of a cascade of 2-ports is the matrix product of the individual ABCD matrices.



$A$  is the ratio between an applied voltage  $v_1$  and the resulting open-circuit voltage  $v_2$  (i.e.  $i_2 = 0$ )  
 $B$  is the ratio between an applied voltage  $v_1$  and the resulting short-circuit current  $i_2$  (i.e.  $v_2 = 0$ )  
 $C$  is the ratio between an applied current  $i_1$  and the resulting open-circuit voltage  $v_2$  (i.e.  $i_2 = 0$ )  
 $D$  is the ratio between an applied current  $i_1$  and the resulting short-circuit current  $i_2$  (i.e.  $v_2 = 0$ )

## *Properties of the ABCD matrix*

$$\begin{bmatrix} S_{1,1} & S_{1,2} \\ S_{2,1} & S_{2,2} \end{bmatrix} = \frac{\begin{bmatrix} A + B/Z_0 - CZ_0 - D & 2(AD - BC) \\ 2 & -A + B/Z_0 - CZ_0 + D \end{bmatrix}}{A + B/Z_0 + CZ_0 + D}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \frac{\begin{bmatrix} (1 + S_{1,1})(1 - S_{2,2}) + S_{1,2}S_{2,1} & Z_0\{(1 + S_{1,1})(1 + S_{2,2}) - S_{1,2}S_{2,1}\} \\ \{(1 - S_{1,1})(1 - S_{2,2}) - S_{1,2}S_{2,1}\}/Z_0 & (1 - S_{1,1})(1 + S_{2,2}) + S_{1,2}S_{2,1} \end{bmatrix}}{2S_{2,1}}$$

- For reciprocal networks, determinant of ABCD matrix AD-BC=1
- For symmetrical networks A = D =  $\pm\sqrt{1+BC}$