

2011-II: Transmission Lines and Antennas


PRINTED ANTENNAS: RECTANGULAR PATCH ANTENNA ANALYSIS AND DESIGN



Javier Leonardo Araque Quijano
Of: 453 – 204, Ext. 14083
jlaraqueq@unal.edu.co
Universidad Nacional de Colombia


1

Printed Antennas

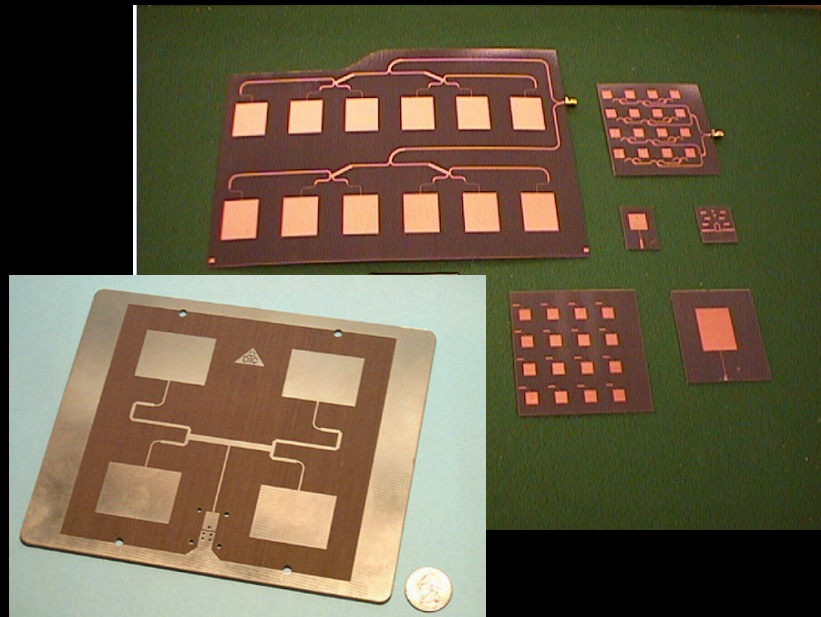



2

Line-fed Rectangular Patch

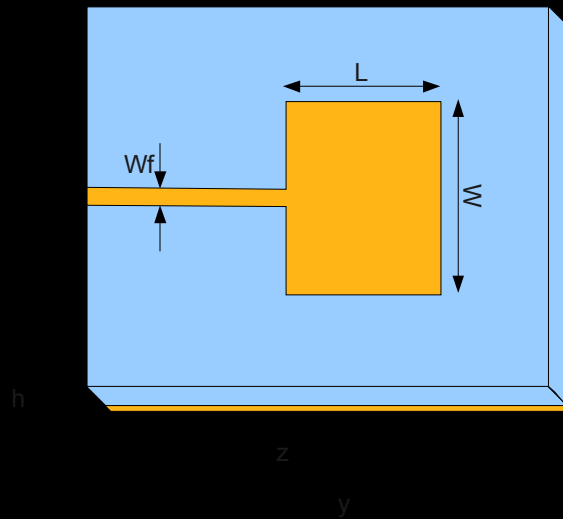


- A grounded substrate is used as support medium, $h \ll \lambda$
- A normal microstrip line is used to feed the antenna ($W_f \ll \lambda$).
- Antenna is a very wide microstrip line ($W \sim \lambda$): wide, open edges allow leaking of guided wave energy into space
- A simple model and analysis will be presented

The Patch as a Transmission Line

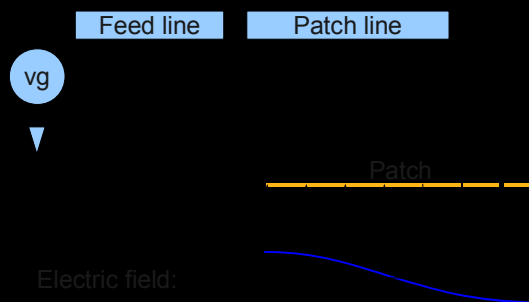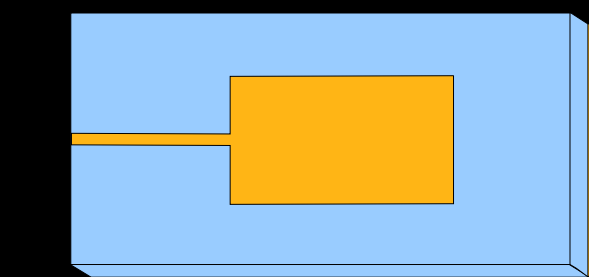

- A simple transmission line model results in a cascade of two lossless lines \rightarrow imaginary Z_{in} .
- Strong discontinuities at patch edges cause leaking of fields (fringing fields):
 - "Loss" (radiation)
 - Capacitive effect at edges (charge accumulation)

Accounting for discontinuities

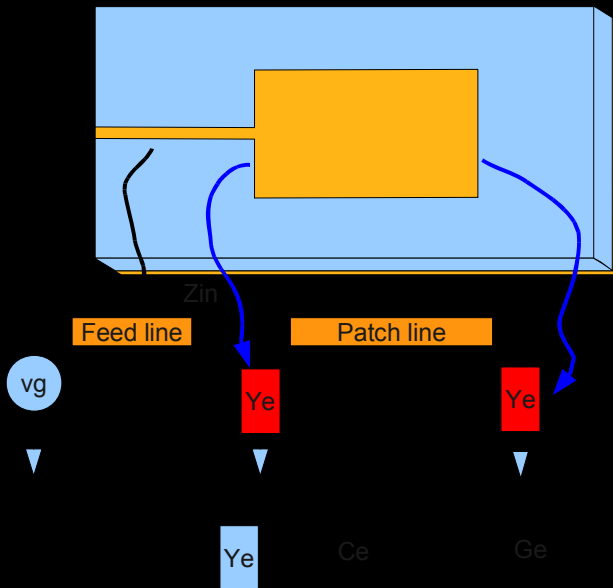

Edge Conductance and Capacitance

- Conductance is obtained from ratio of power radiated by a "slot" to the square modulus of voltage applied:

$$G_e = \frac{2P_{rad}}{|V_0|^2} = \frac{-2 + \cos(X) + X S_i(X) + \frac{\sin(X)}{X}}{120\pi^2}$$

$$X = k_0 W$$

$$S_i(x) = \int_0^x \frac{\sin u}{u} du$$

- Capacitance is most conveniently expressed in terms of the apparent elongation of the patch line using conventional microstrip formulas (real patch length must be $\lambda_g/2$ minus twice this):

$$\frac{\Delta L}{h} = 0.412 \frac{\epsilon_{r,eff} + 0.3}{\epsilon_{r,eff} - 0.258} \cdot \frac{W/h + 0.264}{W/h + 0.8}$$

$$L_{patch} = \frac{\lambda_0}{2\sqrt{\epsilon_{r,eff}}} - 2\Delta L$$

Enhancing the Model

- Computation of G_e above assumes the slot radiates in isolation. Plugging two of these into the model assumes that power adds up, which is not exact since superposition applies to *fields* not power: *fields radiated by these edges interfere in space*, sometimes constructively and sometimes destructively. This effect is accounted by adding a mutual conductance:

$$G_{12} = \frac{1}{120\pi^2} \int_0^\pi \left[\frac{\sin\left(\frac{k_0 W}{2} \cos \theta\right)}{\cos \theta} \right]^2 J_0(k_0 L \sin \theta) \sin^3 \theta d\theta$$

- This model is valid only at resonance or close, as it assumes equi-phase excitation of the "edge antenna elements". Total input impedance is thus computed as follows:

$$R_{in} = \frac{1}{2(G_e + G_{12})}$$




7

Total Antenna Radiation Pattern

$$\underline{e}(\theta, \phi) = -jV_0 4\pi \frac{W}{\lambda_0} \hat{\phi} \sin \theta \operatorname{sinc}\left(\pi \cos \theta \frac{W}{\lambda_0}\right) \cos\left(\pi \frac{L}{\lambda_0} \sin \theta \sin \phi\right)$$


Element factor

Array factor

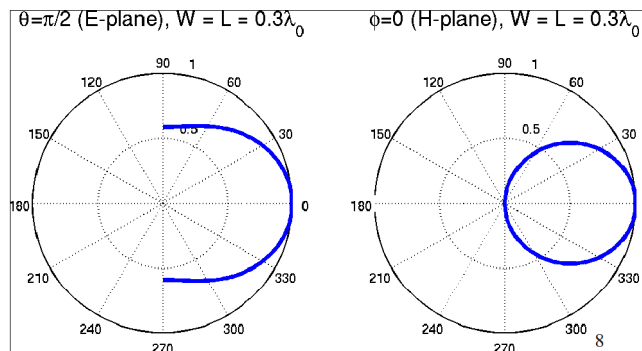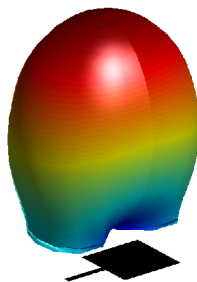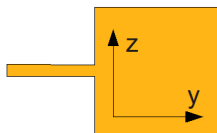

Controlling Patch Input Resistance

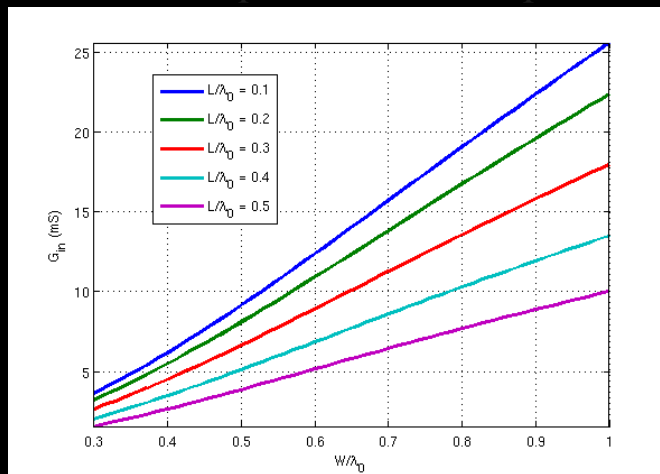
- A wider patch has lower input resistance. Sometimes 50Ω require a too wide patch!



9

Controlling input Resistance (2)

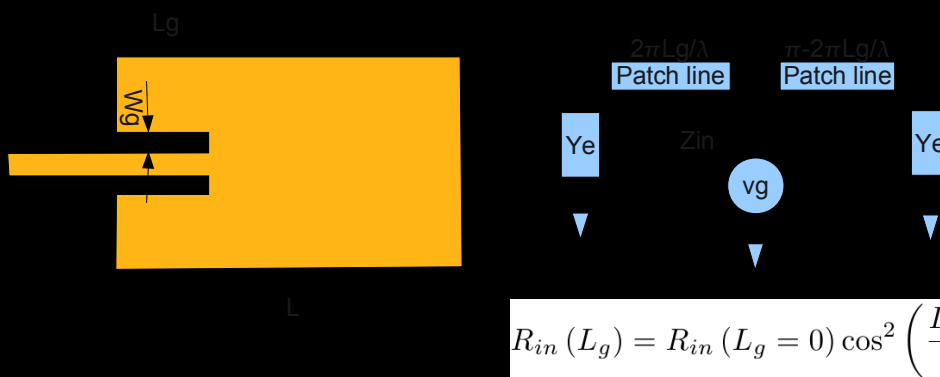- By suitably modifying the feed, different V/I ratio at input terminal are obtained, thus changing input resistance \rightarrow inset feed



- W_g is chosen so that the grounded coplanar waveguide T.L. has the same characteristic impedance as the microstrip line.¹⁰

Patch Design Procedure

Usually one needs to obtain a fixed value for the patch input impedance. Two design procedures can be used:

- Set W to an "optimum" value, then use inset feed to attain the specified impedance.
- Compute W so that input impedance is as given.

11

Design with Inset Feed

- Given h , ϵ_{psr} , Z_{in} :

1. Compute patch width using a rule of thumb value:

$$W_{opt} = \frac{1}{2} \frac{\lambda_0(f_R)}{\sqrt{\epsilon_{average}}} \quad \epsilon_{average} = \frac{1}{2}(\epsilon_r + 1)$$

2. Compute apparent patch elongation ΔL

$$\frac{\Delta L}{h} = 0.412 \frac{\epsilon_{r,eff} + 0.3}{\epsilon_{r,eff} - 0.258} \cdot \frac{W/h + 0.264}{W/h + 0.8}$$

3. Compute patch length considering the above:

$$L = \frac{\lambda_g}{2} - 2\Delta L = \frac{c}{2f\epsilon_{ref}} - 2\Delta L$$

4. Compute resulting R_{in} (from curves or formulas), choose inset dimensions to attain goal R_{in} .

12

Design for R_{in} varying W

- Choose $L/\lambda_0 \approx \frac{1}{2} \frac{1}{\sqrt{\epsilon_r}}$
- Compute W from curves such that Z_{in} is obtained.
- Follow steps 2-4 as in previous case.
- The resulting value for L will be slightly different from the one initially chosen...
- Iterate if necessary with the new value for L